



Image may be representation.  
See specifications for product details.

### LT1396CDD#PBF

Part Number: **LT1396CDD#PBF**  
 Product Description: IC OPAMP CFA 400MHZ 8DFN  
 RoHS Status: Lead free / RoHS Compliant  
 Datasheets: [LT1396CDD#PBF.pdf](#)

Manufacturer/Brand: Link Labs  
 Ship From: Hong Kong  
 Shipment Way: DHL/Fedex/TNT/UPS/EMS

[SUBMIT RFQ](#)

#### Product details

<b>Part Number</b>	LT1396CDD#PBF	<b>Manufacturer</b>	Link Labs
<b>Description</b>	IC OPAMP CFA 400MHZ 8DFN	<b>Lead Free Status / RoHS Status</b>	Lead free / RoHS Compliant
<b>Data sheet</b>	<a href="#">LT1396CDD#PBF.pdf</a>		
<b>Voltage - Supply, Single/Dual (±)</b>	400MHz	<b>Voltage - Input Offset</b>	10µA
<b>Voltage - Breakdown</b>	8-DFN (3x3)	<b>Series</b>	-
<b>RoHS Status</b>	Tube	<b>Polarization</b>	8-WDFDN Exposed Pad
<b>Output Type</b>	-	<b>Orientation</b>	2
<b>Operating Temperature</b>	0°C ~ 70°C	<b>Number of Bits/Stages</b>	1mV
<b>Mounting Type</b>	Surface Mount	<b>Moisture Sensitivity Level (MSL)</b>	1 (Unlimited)
<b>Max Output Power x Channels @ Load</b>	Current Feedback	<b>Manufacturer Standard Lead Time</b>	6 Weeks
<b>Manufacturer Part Number</b>	LT1396CDD#PBF	<b>Expanded Description</b>	Current Feedback Amplifier 2 Circuit 8-DFN (3x3)
<b>Description</b>	IC OPAMP CFA 400MHZ 8DFN	<b>Current - Supply (Main IC)</b>	4 V ~ 12 V, ±2 V ~ 6 V
<b>Current - Supply</b>	4.6mA	<b>Channels per IC</b>	80mA
<b>-3db Bandwidth</b>	800 V/µs		

#### Related Products

 <b>LT1395CS8#PBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8SO Download: <a href="#">LT1395CS8#PBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1395CS6#TRMPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ TSOT23-6 Download: <a href="#">LT1395CS6#TRMPBF.pdf</a>	<a href="#">RFQ</a>
 <b>LT1397CDE#PBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 14DFN Download: <a href="#">LT1397CDE#PBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1395CS6#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ TSOT23-6 Download: <a href="#">LT1395CS6#TRPBF.pdf</a>	<a href="#">RFQ</a>
 <b>LT1395CS8#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8SO Download: <a href="#">LT1395CS8#TRPBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1395CS5#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ TSOT23-5 Download: <a href="#">LT1395CS5#TRPBF.pdf</a>	<a href="#">RFQ</a>
 <b>LT1396CMS8#PBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8MSOP Download: <a href="#">LT1396CMS8#PBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1396CMS8#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8MSOP Download: <a href="#">LT1396CMS8#TRPBF.pdf</a>	<a href="#">RFQ</a>
 <b>LT1396CDD#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8DFN Download: <a href="#">LT1396CDD#TRPBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1395CS6#TRM</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ TSOT23-6 Download: <a href="#">LT1395CS6#TRM.pdf</a>	<a href="#">RFQ</a>
 <b>LT1396CS8#TRPBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8SO Download: <a href="#">LT1396CS8#TRPBF.pdf</a>	<a href="#">RFQ</a>	 <b>LT1396CS8#PBF</b> Manufacturers: ADI (Analog Devices, Inc.) Description: IC OPAMP CFA 400MHZ 8SO Download: <a href="#">LT1396CS8#PBF.pdf</a>	<a href="#">RFQ</a>

#### Related tags

Link Labs LT1396CDD#PBF  
 LT1396CDD#PBF Price  
 LT1396CDD#PBF PDF Datasheet  
 LT1396CDD#PBF Stock  
 Link Labs LT1396CDD#PBF  
 Link Labs LT1396CDD#PBF

LT1396CDD#PBF Distributor  
 LT1396CDD#PBF Pictures  
 LT1396CDD#PBF Download Datasheet  
 Buy LT1396CDD#PBF  
 Link Labs Supplier  
 Link Labs Inc. LT1396CDD#PBF

LT1396CDD#PBF Supplier  
 LT1396CDD#PBF Image  
 LT1396CDD#PBF Datasheet  
 Buy Link Labs LT1396CDD#PBF  
 Link Labs Distributor